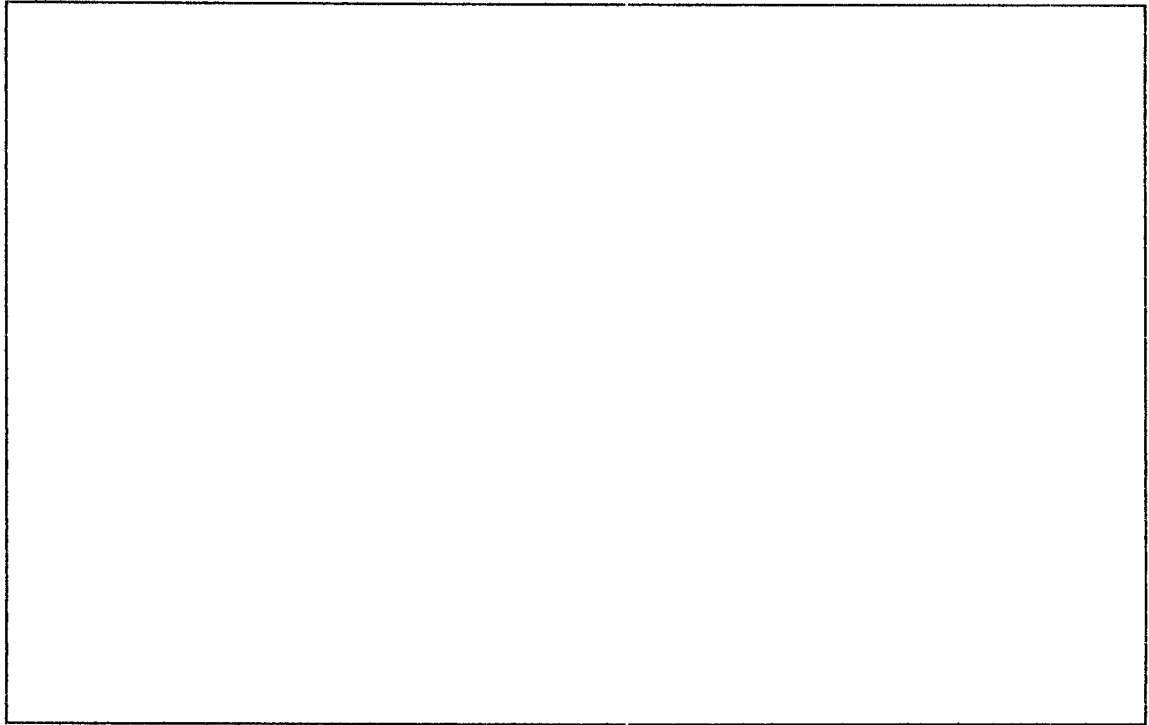


Name _____


Basic Electronics Sign Project #4

1. On this sheet design a sign out of L. E. D.'s that not only flashes, but part of the sign must remain on while in operation. Show how they will be soldered together in parallel (second box). Remember "The foil side is opposite of the component side."
2. I will supply you with 30 red, yellow and green L. E. D.'s . You must use your 555 flasher circuit to power your sign.
3. You must fit your sign on a piece of 4"x6" Masonite.

DESIGN
Component
Side



Foil side

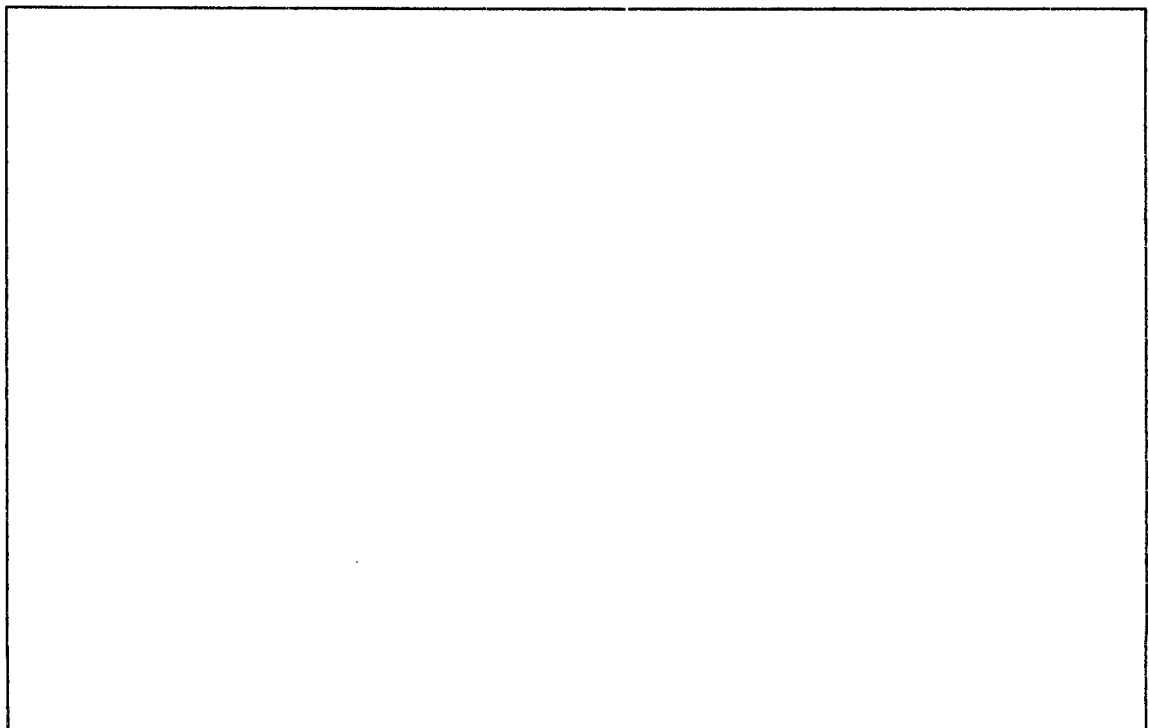

Parallel CIRCUIT

Show holes for L.E.D.'s remember space them 1/8" apart.

555 FLASHER

PROJECT #4

Materials List:

- 1 - 555 IC
- 1 - 8 pin IC socket
- 2 - LEDs
- 1 - 4.7K Ω
- 1 - 75K Ω

- 1 - 15 Ω
- 1 - 10 μ F
- 1 - 9-Volt battery clip

NOTE:

The board size
is 1 1/2" x 2"

