

NAME: _____

ASSIGNMENT: DESIGN YOUR OWN CIRCUIT BOARD USING THE FOLLOWING INFORMATION.

MATERIALS:

- 2" x 2" Circuit Board
- 4.3KΩ Resistor
- 82KΩ Resistor
- .01μF Capacitor
- 2N3904 Transistor
- 2N3906 Transistor
- Speaker
- 9 Volt Battery Clip

