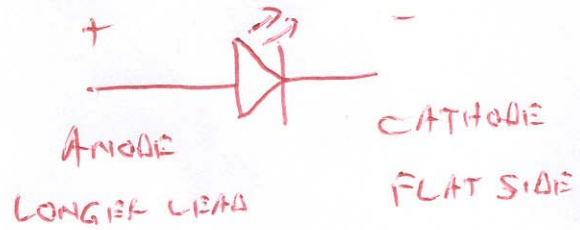


# BASIC ELECTRONICS

## PROJECT #2: (Polarity/Continuity Tester)

### SCHEMATIC



### MATERIALS:

- 4- 6" wires
- 1- Battery clip
- 2- Red LEDs
- 1- Green LED
- 1- 820Ω Resistor
- 1- 100Ω Resistor
- 1- 1 1/2" x 1 1/2" piece of circuit board

